

1.
 - i. (a)
 - ii. 因 if 之後沒有 else，且 Q 也沒有先給予一個值，所以為了讓 $Q=Q$ ，硬體部分會多合成一個 latch

2. (a) minimum cover: $B'D + CD$

(b) P1: 10 10 11 11



P2: 10 11 11 01

P3: 11 10 11 01

P4: 11 11 01 01



(c)

(1) $A < B < C < D$

  

$A > B > C > D$

0, 1, 2, 3, 5, 7, 9, 11, 15

  

(d) position cube

pro: 運算快, 資料結構簡單

con: minimum cover 難找

ROBDD

pro: tree 唯一

con: 需要較大的記憶體儲存


3.

(a)

	a	b	c	d	e	g
ace	1	0	1	0	1	0
bce	0	1	1	0	1	0
de	0	0	0	1	1	0
g	0	0	0	0	0	1
ad	1	0	0	1	0	0
bd	0	1	0	1	0	0
cde	0	0	1	1	1	0
ge	0	0	0	0	1	1
a	1	0	0	0	0	0
b	0	1	0	0	0	0

co-kernel: ce, de

(b)

 

$X = Az + de + g$ before: $9 + 9 + 2 = 20$ literals, after: $5 + 5 + 2 + 2 = 14$ literals

$y = zd + dA + ge = d(A + z) + ge$

$z = a + b$

$A = ce$

(c)

從 two-level circuit \rightarrow multi-level circuit


Advantage: 可共用 gates, area \downarrow

Disadvantage: Multi-level circuit delay 變長

合併後的新 variable 也會位 literal 數目

所以不一定能使 literal 數下降

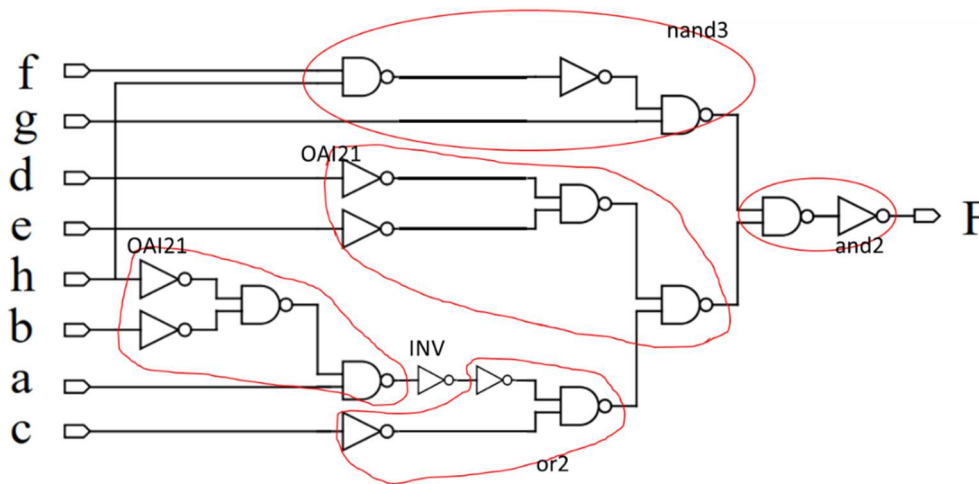4. Split: split the fanouts of a gate into several parts. Each part is driven with a copy of the original gate, loading decrease -> timing improve
Critical path collapsing: reduce the depth of logic networks, length of critical path decrease -> timing improve
Different: split 沒有改變深度，而 Critical path collapsing 則會
5. i. supply voltage/ threshold voltages/ frequency
ii. Power Gating, Power gating design can reduce the leakage power when the block is powered off/ Power gating further reduces the standby power,
iii. Not always. Require longer wakeup time in the WAKE event, area increasing or IR drop...
- 6.



Minimum gate count = 6

7.

(a) gate	delay(ps)
1	4
2	2
3	12.5
4	6.65
5	5.65
6	9.44

(b)

longest sensitizable path:


$G_1 \rightarrow G_3 \rightarrow G_4 \rightarrow G_6$

path delay = $4 + 12.5 + 5.65 + 9.44$

= 31.59 ps *

8.

(a)

 

(b)

critical path 上的 propagation delay 變小,
⇒ clock period 減小 (frequency 提高)